컴퓨터공학 기초 실험2

Lab #9

Multiplier

MULTIPLIER

Multiplier

➤ Multiplier 는 multiplicand(피승수)와 multiplier(승수)를 곱하여 결과값을 도출하는 hardware이다.

> Features

✓ Multiplicand와 multiplier의 각각의 bit length는 64bits 이며, 곱의 결과값은 128 bits이다.

Binary Multiplication

$$\triangleright$$
 Ex) 5 x 3 = 15

A	0101	(5) Multiplicand
X	X 0011	(3) Multiplier
	0101	
	0101	Portial products
	0000	Partial products
	0000	
	0001111	(15)

Binary Multiplication

$$\triangleright$$
 Ex) 5 x -3 = -15

A		(5) Multiplicand
X	X 1101	(-3) Multiplier
	0101	
	0000	
	0101	Partial products
	0101	
	1011	
	11110001	(-15)

Multiplier가 음수인 경우 맨 마지막에 multiplicand의 보수 값을 더해준다.

> Rule of booth multiplication

x_i	x_{i-1}	Operation	Description
0	0	Shift only	String of zeros
0	1	Add and shift	End of a string of ones
1	0	Subtract and shift	Beginning of a string of ones
1	1	Shift only	String of ones

Ex)
$$7 \times -7 = -49$$

A 0111 (7)
X 10010 (-7)

\mathbf{U}	${f V}$	\mathbf{X}	X-1
0000	0000	1001	0
		Subt	raction

LSB(least significant bit)의 오른쪽에는 0비트가 있다고 가정하고 Y를 구함 $\{x_ix_{i-1}\}=10_{(2)} \Rightarrow Y=\overline{1}$

Ex)
$$7 \times -7 = -49$$


A 0111 (7)
X 10010 (-7)

$$0000 \\ +1001 \\ \hline 1001$$

${f U}$	${f V}$	\mathbf{X}	X-1
0000	0000	1001	0
1001			
1001	0000		

 \Rightarrow Ex) 7 x -7 = -49 A 0111 (7)

X 10010 (-7)

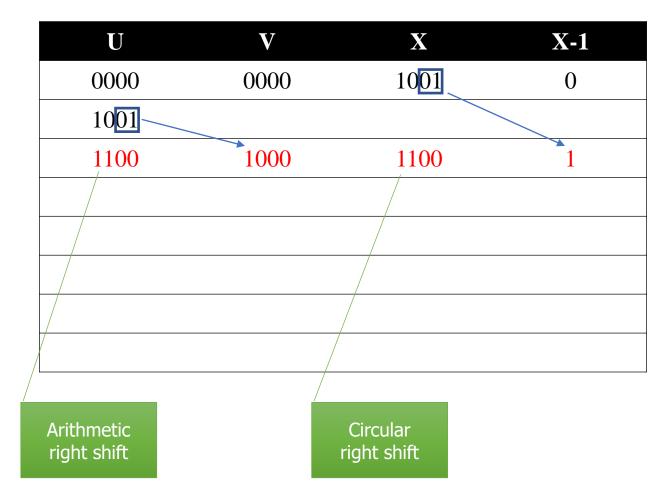

Ex)
$$7 \times -7 = -49$$

A 0111 (7)
X 10010 (-7)

${f U}$	${f V}$	\mathbf{X}	X-1
0000	0000	1001	0
1001			
1100	1000	110 <mark>0</mark>	1
0111		Ado	dition
0011	1000		

Ex)
$$7 \times -7 = -49$$

A 0111 (7)
X 10010 (-7)

U	V	X	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	0110	0

Ex)
$$7 \times -7 = -49$$

A 0111 (7)
X 10010 (-7)

U	V	X	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	011 <mark>0</mark>	0
		Sh	nift

Ex)
$$7 \times -7 = -49$$

A 0111 (7)
X 10010 (-7)

${f U}$	${f V}$	X	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	0110	0
0000	1110	0011	0

Ex)
$$7 \times -7 = -49$$
A 0111 (7)
X 10010 (-7)

${f U}$	${f V}$	\mathbf{X}	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	0110	0
0000	1110	0011	0
		Subti	raction

$$\triangleright$$
 Ex) 7 x -7 = -49

A 0111 (7)

X 10010 (-7)

 $0000 \\ +1001 \\ \hline 1001$

${f U}$	\mathbf{V}	X	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	0110	0
0000	1110	0011	0
1001			
1001	1110		

Ex)
$$7 \times -7 = -49$$

A 0111 (7)
X 10010 (-7)

${f U}$	${f V}$	\mathbf{X}	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	0110	0
0000	1110	0011	0
1001			
1100	1111	1001	1

$$\triangleright$$
 Ex) 7 x -7 = -49

A 0111 (7)

X = 10010 (-7)

11001111 (-49)

U	V	X	X-1
0000	0000	1001	0
1001			
1100	1000	1100	1
0111			
0001	1100	0110	0
0000	1110	0011	0
1001			
1100	1111	1001	1

4 clock cycle after, STOP

Radix-4 Booth Multiplication

> Rule of radix -4 booth multiplication

x_i	x_{i-1}	x_{i-2}	Operation	y_i	y_{i-1}	У
0	0	0	0+0=0	0	0	0
0	0	1	0+A=A	0	1	+1
0	1	0	2A-A=+A	0	1	+1
0	1	1	2A+0=2A	1	0	+2
1	0	0	-2A+0=-2A	-1	0	-2
1	0	1	-2A+A=-A	0	-1	-1
1	1	0	0-A=-A	0	-1	-1
1	1	1	0+0=0	0	0	0

PRACTICE

Project Properties

- > New Project Wizard
 - ✓ Project name : multiplier
 - ✓ Family & Device: Cyclone V 5CSXFC6D6F31C6(밑에서 6번째)

Pin Description

Direction	Port name	Description		
nniif -	clk	Clock		
	reset_n	Active low reset		
	multiplier[63:0]	승수		
	multiplicand[63:0]	피승수		
	op_start	Start operation		
	op_clear	Clear operation		
Output	op_done	Done operation		
	result[127:0]	Multiplier result		

Assignment 9

- > Report
 - ✓ 자세한 사항은 homework & practice document 참고
- > Submission
 - ✓ Soft copy
 - 강의 후 2주 뒤 제출
 - Delay는 2일까지

Q&A

THANK YOU